



**North South University**  
**Department of Electrical & Computer Engineering**  
**LAB REPORT-**

Course Code: CSE 231

Course Title: Digital Logic Lab

Section: 9

Lab Number: 5

Experiment Name:

Binary Arithmetic

Experiment Date: 1 May 2024

Date of Submission: 15 May 2024

Submitted by Group Number: 02

Group members

Name	ID	Obtained Mark Simulation [5]	Obtained Mark Lab Report [15]
1 M.A. Rayhan Sharif Ratsun	2222472042		
2.			
3.			
4.			

Course Instructor: Omar Ibne Shahid

Submitted To: Pritthika Dhar

## 1: LAB 5 : Binary Arithmetic

### 2A. Objectives

- Minimize combinational logic circuits using Karnaugh map.
- Learn various numerical representation system.
- Implement circuits using 1st and 2nd canonical minimal forms.
- Implement circuits using universal logic.

3. Theory : Binary adder performs binary addition on the A and B input and the carry output CO. It generates a 4 bit sum and a carry out C4. It can be Half Adder which is a fundamental building block of a binary adder. It adds two single digit binary numbers and produces two output. The sum (S) and the carry (C). ICs like the 7400 series often contain integrated half adder circuits. Another one is full adder, while a half adder can add two bits, it cannot account for a carry from a previous addition. A full adder, built using multiple half adder and additional logic gates, can handle three inputs: two bits to be added and a carry from the previous lower significant bit addition.

Two 7483 ICs can be cascaded to form an 8-bit

ripple through -carry adder. The lower 4-bits of each number is used as input for the first 7483 and the output carry is connected to the input carry of the next 7483. The higher 4 bits of the sum and the second one provides the upper 4-bits.

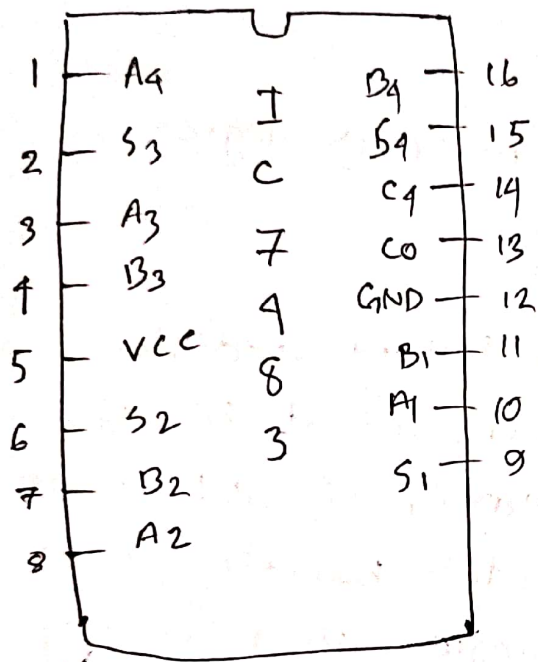


Figure: Pinout of IC 7483



Apparatus:

### Experiment 1: Binary Adder - Subtractor

- Trainer Board
- 1x IC 7483 4-bit binary Adder
- 1x IC 7486 quadruple 2-input x-OR gates

### Experiment - 2 : Ripple - Through - Carry Adder

- Trainer Board
- 2x IC 7483 4-bit binary Adder

### Experiment - 3 : BCD Adder

- Trainer Board
- 2x IC 7483 4 bit binary adder
- 1x IC 7408 quadruple 2-input AND gate
- 1x IC 7432 quadruple 2-input OR gate

### Experiment Data: Binary Adder - Subtractor

Operation	M	A	B	C <sub>4</sub>	S <sub>4</sub> S <sub>3</sub> S <sub>2</sub> S <sub>1</sub>
7+5	0	0111	0101	0	1 1 0 0
4+6	0	0100	0110	0	1 0 1 0
9+11	0	1001	1011	1	0 1 0 0
15+15	0	1111	1111	1	1 1 1 0
7-5	1	0111	0101	0	0 0 1 0
4-6	1	0100	0110	1	1 1 1 0
11-2	1	1011	0010	0	1 0 0 1
15-15	1	1111	1111	0	0 0 0 0

Table: F.1.1

# Experimental Data (Ripple - Through - Carry - Adder)

Operation	A	B	overflow error	Sum
7+5	00000111	0000 00101	0	00001100
18+19	0001 0010	0001 0011	0	0010 0101
72+83	0100 1000	0101 0011	0	1001 1011
129+255	1000 0001	1111 1111	1	1000 0000

## Experimental Data (BCD sum)

Binary		Sum				BCD Sum			
K	Z <sub>8</sub>	Z <sub>4</sub>	Z <sub>2</sub>	Z <sub>1</sub>	C	S <sub>8</sub>	S <sub>4</sub>	S <sub>2</sub>	S <sub>1</sub>
0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	0	0	1	0
0	0	0	1	1	0	0	0	1	1
0	0	1	0	0	0	0	1	0	0
0	0	1	0	1	0	0	1	0	1
0	0	1	1	0	0	0	1	1	0
0	0	1	1	1	0	0	1	1	1
0	1	0	0	0	0	1	0	0	0
0	1	0	0	1	0	1	0	0	1
0	1	0	1	0	1	0	0	0	0
0	1	0	1	1	1	0	0	0	1
0	1	1	0	0	1	0	0	1	0
0	1	1	0	1	1	0	0	1	1
0	1	1	1	0	1	0	1	0	0
0	1	1	1	1	1	0	1	0	1
1	0	0	0	0	1	0	1	1	0
1	0	0	0	1	1	0	1	1	1
1	0	0	1	0	1	1	0	0	0
1	0	0	1	1	1	1	0	0	1



## Experimental Procedure:

### Binary Adder Subtractor:

1. First we select four switches to represent the bits of input A and another four more binary switches to represent the bits of input B.
2. Then we select another switch for the mode chosen.
3. Then we construct the circuit according to the pin details in the circuit diagram section.
4. We chose four LEDs, to view the output sum and another LED for the output carry.
5. We test the circuit with the data in table for the BCD Sum.

### BCD Adder:

1. First we complete table F.2.1 and F.2.2 for the BCD sum.
2. Then we construct the circuit.
3. We use the first adder output as the input of the second adder.
4. We built the circuit according to the pin details shown in circuit D.2.2.
5. Then we test the circuit with data in table: F.2.2

# Circuit Diagram :


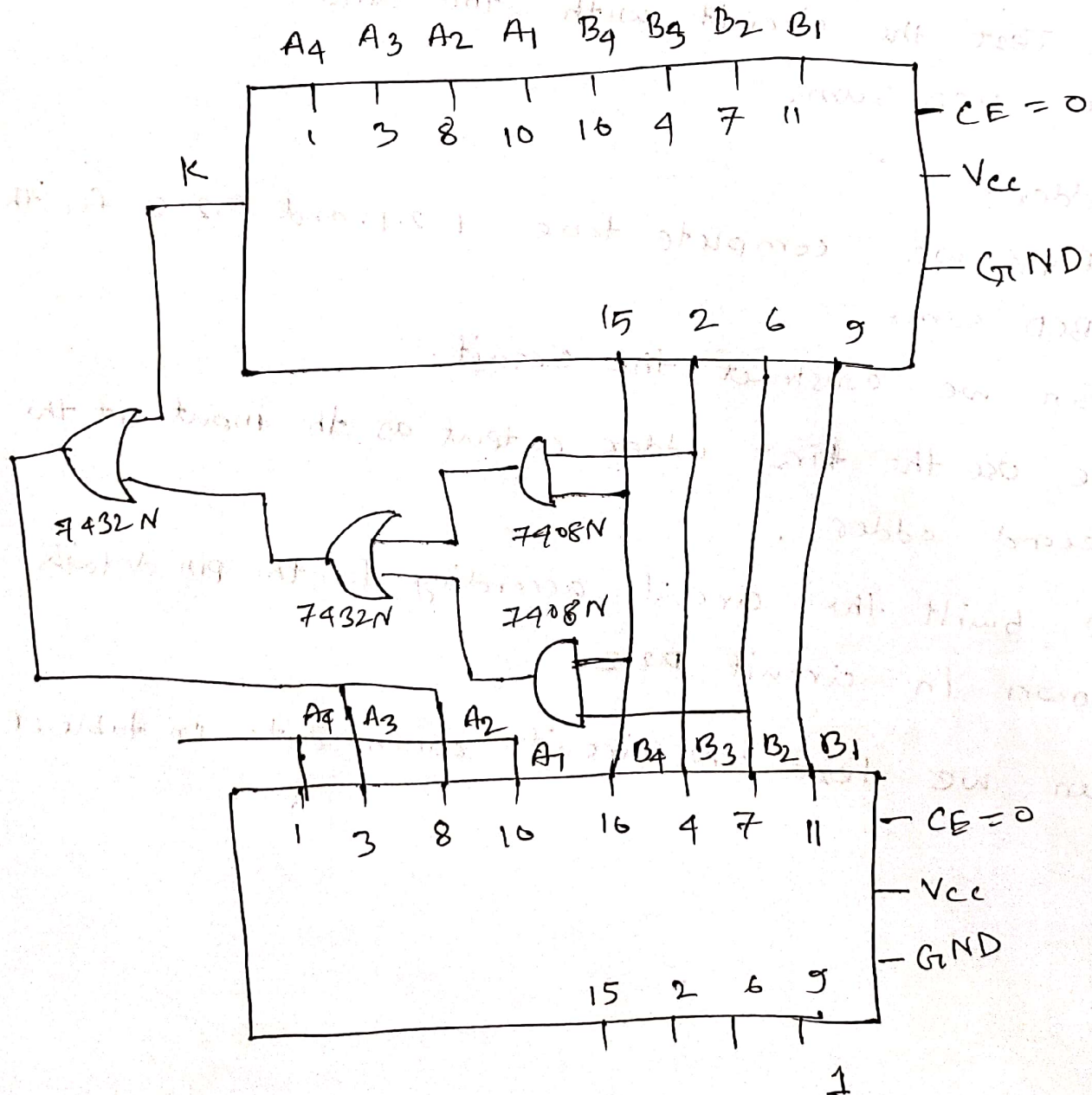


Figure : D.2.1; 4-bit Adder circuit

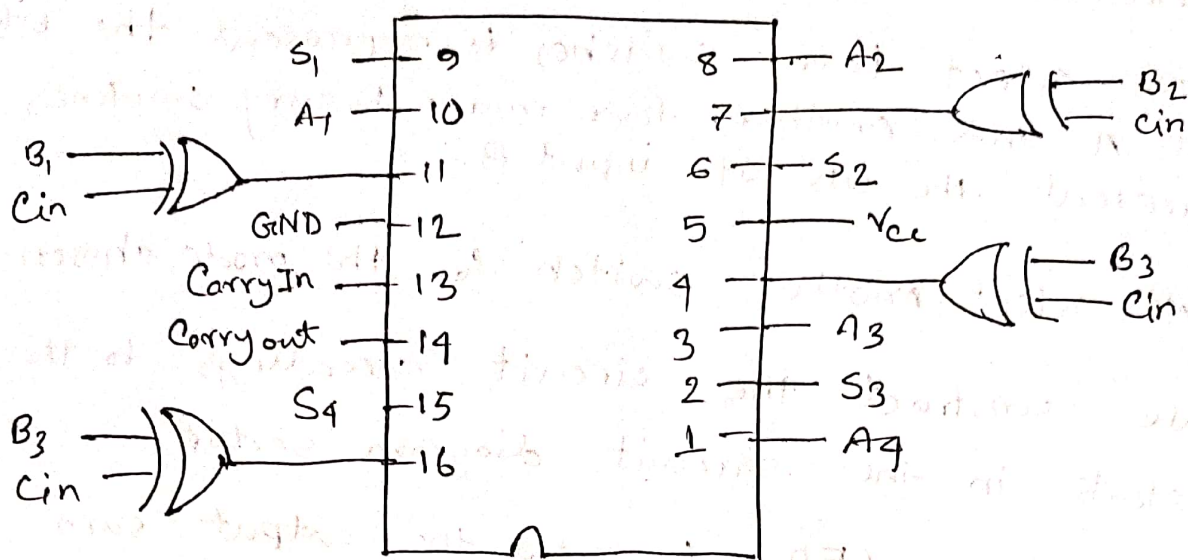

Operation	A	B	Overflow Carry	Sum
9+0	1001	0000	0	1001
9+1	1001	0001	1	0000
9+2	1001	0010	1	0001
9+3	1001	0011	1	0010
9+4	1001	0100	1	0011
9+5	1001	0101	1	0100
9+6	1001	0110	1	0101
9+7	1001	0111	1	0110
9+8	1001	1000	1	0111
9+9	1001	1001	1	1000

table: F.2.2

### Result:

After implementation of our circuits, we test it with the data table F.1.1, F.2.1, and we get the exact output as the table.

### Question and Answer:

01. In this experiment, we use XOR gates for the input of B to converted in the first complements and then we use the M bit as carryin, to convert the B to the second complements.



According to the truth table, when M bit is 0, the inputs of B will not change. And when the M bit is 1, inputs of B will convert. We know that for the subtractor, we need to convert the negative number to second complements, then we can add and get the final result.

input		output
A	B	
0	0	0
0	1	1
1	0	1
1	1	0

X-OR Gate

Discussion: Through this experiment, we

understand the concept of binary addition and subtraction. We can use half and Full Binary Adders. We can do addition and subtraction by using this adder. We also learn the concept of BCD sum. In the first part, our circuit was unable to do subtractor, but then we identify that the adder IC was damaged. Then we replace it and get the accurate result. In the second part we didn't get face any problem and complete within time. In short we learned about the adder and subtractor circuits.