



**North South University**  
**Department of Electrical & Computer Engineering**  
**LAB REPORT- 02**

Course Code: CSE 231

Course Title: Digital Logic

Section: 09

Lab Number: 02

Experiment Name:

Combinational Logic Design

Experiment Date: 13.03.2024

Date of Submission: 20.03.2024

Submitted by Group Number: 02

Group members:

Name	ID	Obtained Mark Simulation [5]	Obtained Mark Lab Report [15]
1. Shakil Ahmed	2221453042		
2. Munem Bulbul	2221314642		
3. Sudipto Roy	2222756042		
4. MD Rayhan Sharif Rafsun	2222472042		

Course Instructor: Omer Ibne Shahid (OISD)

Submitted To: Prithika Dhar

## Experiment Name: Combinational Logic Design

- Objectives :
- Becoming familiarize with the analysis of combinational logic network
  - Learning the implementation of networks using two canonical forms.
  - Devise combination circuit using universal logic
  - Acquaint with basic binary arithmetic circuits



Apparatus : Trainer Board, 1x IC 7411 Triple 3-input AND gates, 1x IC 7432 Triple 3-input OR gates, 1x IC 7404 Hex Inverters

- Theory :
- Minterm for each combination of the variables that produce a 1 in the function and taking the 'OR' of all those terms.
- minterm in variables = product of  $n$  literals in which each variable appears exactly once either in T or F form.
  - Each minterm has value 1 for exactly one combination values of variables. example:  $ABC(111) \Rightarrow m_7$ .
  - A function can be written as a sum of minterms, referred to as a minterm expansion or a standard sum of products.

- Maxterm for each combination of variables that produces a 0 in the function and then taking the AND of all those terms
- maxterm of  $n$  variables = sum of  $n$  literals in which each variable appears exactly once in T or F form, but not in both
  - Each maxterm has a value of 0 for exactly one combination of values of variables. example:  $A+B+C(001) \Rightarrow M_1$  (value is 0)
  - Function can be written as a product of maxterms, which is referred to as a maxterm expansion or standard product of sum

Canonical forms: The technique that is used to represent the mathematical entities or matrix in its standard form is termed as canonical form. The term canonicalization is also known as standardization or normalization with respect to the equivalence relation.

### Circuit Diagram:

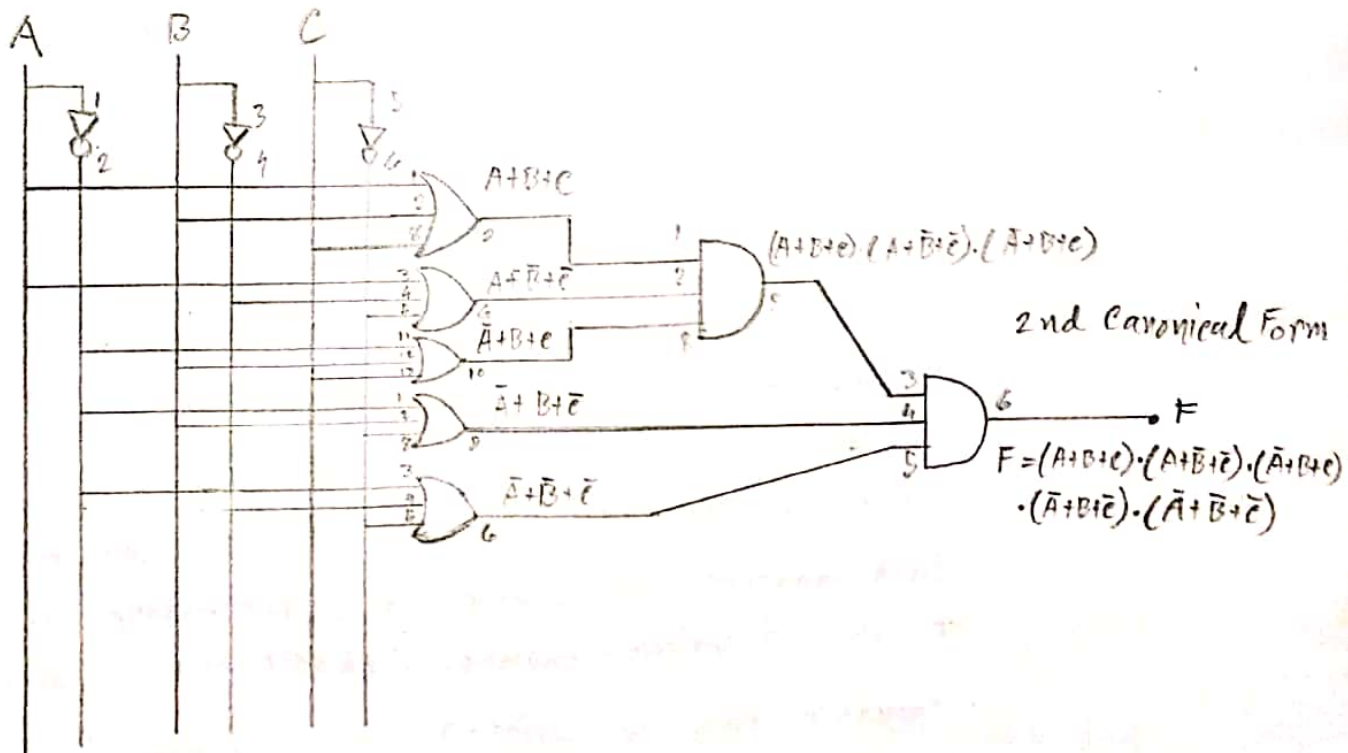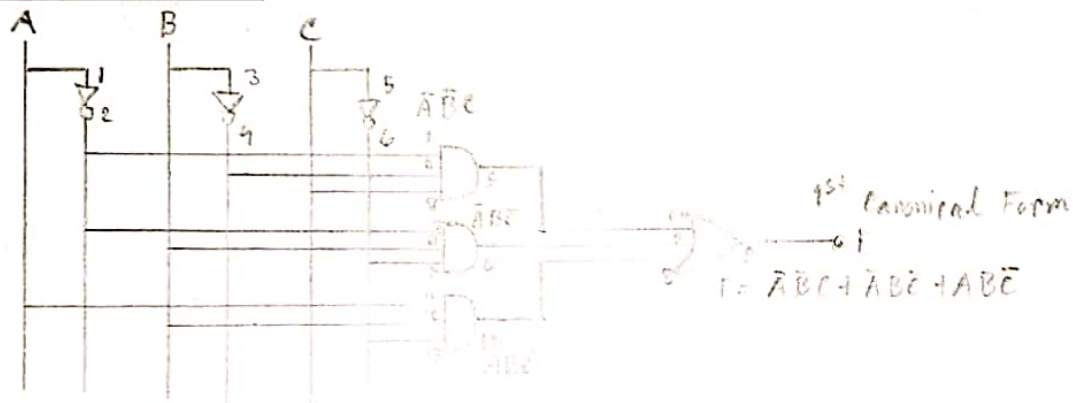

Experimental Procedure: All the minterms of three inputs ABC:

$\bar{A}\bar{B}\bar{C}(m_0), \bar{A}\bar{B}C(m_1), \bar{A}B\bar{C}(m_2), \bar{A}BC(m_3), A\bar{B}\bar{C}(m_4), A\bar{B}C(m_5), AB\bar{C}(m_6), ABC(m_7)$ .

All the Max terms for three input ABC:

$A+B+C(M_0), A+B+\bar{C}(M_1), A+\bar{B}+C(M_2), A+\bar{B}+\bar{C}(M_3), \bar{A}+B+C(M_4), \bar{A}+B+\bar{C}(M_5), \bar{A}+\bar{B}+C(M_6), \bar{A}+\bar{B}+\bar{C}(M_7)$

In the logic / Trainer board we will set up the connections like for 1st canonical form minterms will be  $m_1, m_2, m_6$  which will give us 1 output. And for 2nd canonical form  $M_0, M_3, M_4, M_5$  and  $M_7$  will give us true output.

Experimental Data Table:

Input Reference	A B C	F	Minterm	Max term
0	0 0 0	0	$\bar{A}\bar{B}\bar{C} (m_0)$	$A+B+C (M_0)$
1	0 0 1	1	$\bar{A}\bar{B}C (m_1)$	$A+B+\bar{C} (M_1)$
2	0 1 0	1	$\bar{A}B\bar{C} (m_2)$	$A+\bar{B}+C (M_2)$
3	0 1 1	0	$\bar{A}BC (m_3)$	$A+\bar{B}+\bar{C} (M_3)$
4	1 0 0	0	$A\bar{B}\bar{C} (m_4)$	$\bar{A}+B+C (M_4)$
5	1 0 1	0	$A\bar{B}C (m_5)$	$\bar{A}+B+\bar{C} (M_5)$
6	1 1 0	1	$AB\bar{C} (m_6)$	$\bar{A}+\bar{B}+C (M_6)$
7	1 1 1	0	$ABC (m_7)$	$\bar{A}+\bar{B}+\bar{C} (M_7)$

Truth table to a combinational circuit

	Shorthand Notation	Function
1 <sup>st</sup> Canonical Form	$F = \sum (m_1, m_2, m_6)$	$F = \bar{A}\bar{B}C + \bar{A}B\bar{C} + AB\bar{C}$
2 <sup>nd</sup> Canonical Form	$F = \prod (M_0, M_3, M_4, M_5, M_7)$	$F = (A+B+C)(A+\bar{B}+\bar{C})(\bar{A}+\bar{B}+C)(\bar{A}+B+\bar{C})(\bar{A}+\bar{B}+\bar{C})$

1<sup>st</sup> and 2<sup>nd</sup> canonical forms of the combinational circuit



Discussion: In this experiment we learned about the two canonical forms and how they work. We also learned that two different circuit can give same result if arranged properly. For this experiment we had 1 IC ~~7404~~ Hex Inverter (Not gate) 1 IC with three input AND gate ~~7411~~ 4073 and two IC with three input OR gate 4075. For minterm we didn't face any problem as it only required one AND and one OR and a Hex Inverter. But in Maxterm we had to use two OR IC gate and the circuit was very complex for that reason it took more time than expected.

While using two OR gates we used 1 OR IC for three Maxterm then connected output to AND gate input while the two other OR output from the other OR IC we connected these inputs to second AND input and got the expected output.

Wiring the circuit in maxterm was quite challenging because we needed to connect a lot of gates. We also needed to use a lot of wires. and Alhamdulillah the experiment was working out. All our equipment were working perfectly. We did it on first try and did not face that much trouble in this experiment.

**North South University**  
**Department of Electrical and Computer Engineering**  
**CSE 231L: Digital Logic Design Lab**  
**Lab 02: Combinational Logic Design**

**A. Objectives**

- Familiarize with the analysis of combinational logic network.
- Learn the implementation of networks using the two canonical forms.
- Devise combinational circuits using universal logic.
- Acquaint with basic binary arithmetic circuits –the half and full adders.

**B. Theory**

Concise theory pertinent to lab experiments to go here to aid students in performing experiments with minimal supervision. For example, topics for this lab should include definition and steps to:

Analysis of combinational logic design Min terms and max terms

Canonical Forms

Universal gates – bubble pushing, De Morgan's theorem.

**C. Experiment 1: Analysis of a Combinational Logic Circuit**

**C.1. Equipments:**

- Trainer Board
- 1 x IC 7411 Triple 3-input AND gates
- 1 x IC 7432 Quadruple 2-input OR gates
- 1 x IC 7404 Hex Inverters (NOT gates)

**C.2. Procedure**

Input Reference	A B C	F	Min term	Max term
0	0 0 0	0	$\bar{A}\bar{B}\bar{C}$ ( $m_0$ )	$A+B+C$ ( $M_0$ )
1	0 0 1	1	$\bar{A}\bar{B}C$ ( $m_1$ )	$A+B-\bar{C}$ ( $M_1$ )
2	0 1 0	1	$\bar{A}B\bar{C}$ ( $m_2$ )	$\bar{A}+B+C$ ( $M_2$ )
3	0 1 1	0	$\bar{A}BC$ ( $m_3$ )	$A+\bar{B}+\bar{C}$ ( $M_3$ )
4	1 0 0	0	$AB\bar{C}$ ( $m_4$ )	$A+\bar{B}+C$ ( $M_4$ )
5	1 0 1	0	$AB\bar{C}$ ( $m_5$ )	$\bar{A}+\bar{B}+\bar{C}$ ( $M_5$ )
6	1 1 0	1	$ABC$ ( $m_6$ )	$\bar{A}+B+C$ ( $M_6$ )
7	1 1 1	0	$ABC$ ( $m_7$ )	$\bar{A}+\bar{B}+\bar{C}$ ( $M_7$ )

Table C.1 Truth table to a combinational circuit

1. Write down all the min terms and max terms of three inputs ABC in Table C.1.
2. Write down the function F in 1<sup>st</sup> and 2<sup>nd</sup> Canonical Forms in Table C.2.

	Shorthand Notation	Function
1 <sup>st</sup> Canonical Form	$F = \Sigma (m_1, m_2, m_6)$	$F = \bar{A}\bar{B}C + \bar{A}B\bar{C} + ABC$
2 <sup>nd</sup> Canonical Form	$F = \Pi (M_0, M_3, M_4, M_5, M_7)$	$F = (A+B+C) \cdot (A+\bar{B}+\bar{C}) \cdot (\bar{A}+B+C) \cdot (\bar{A}+\bar{B}+\bar{C}) \cdot (\bar{A}+\bar{B}+\bar{C})$

Table C.2 1<sup>st</sup> and 2<sup>nd</sup> canonical forms of the combinational circuit of Table C.1

3. Draw the circuits in the space provided below, clearly indicating the pin numbers corresponding to the relevant

ICs.

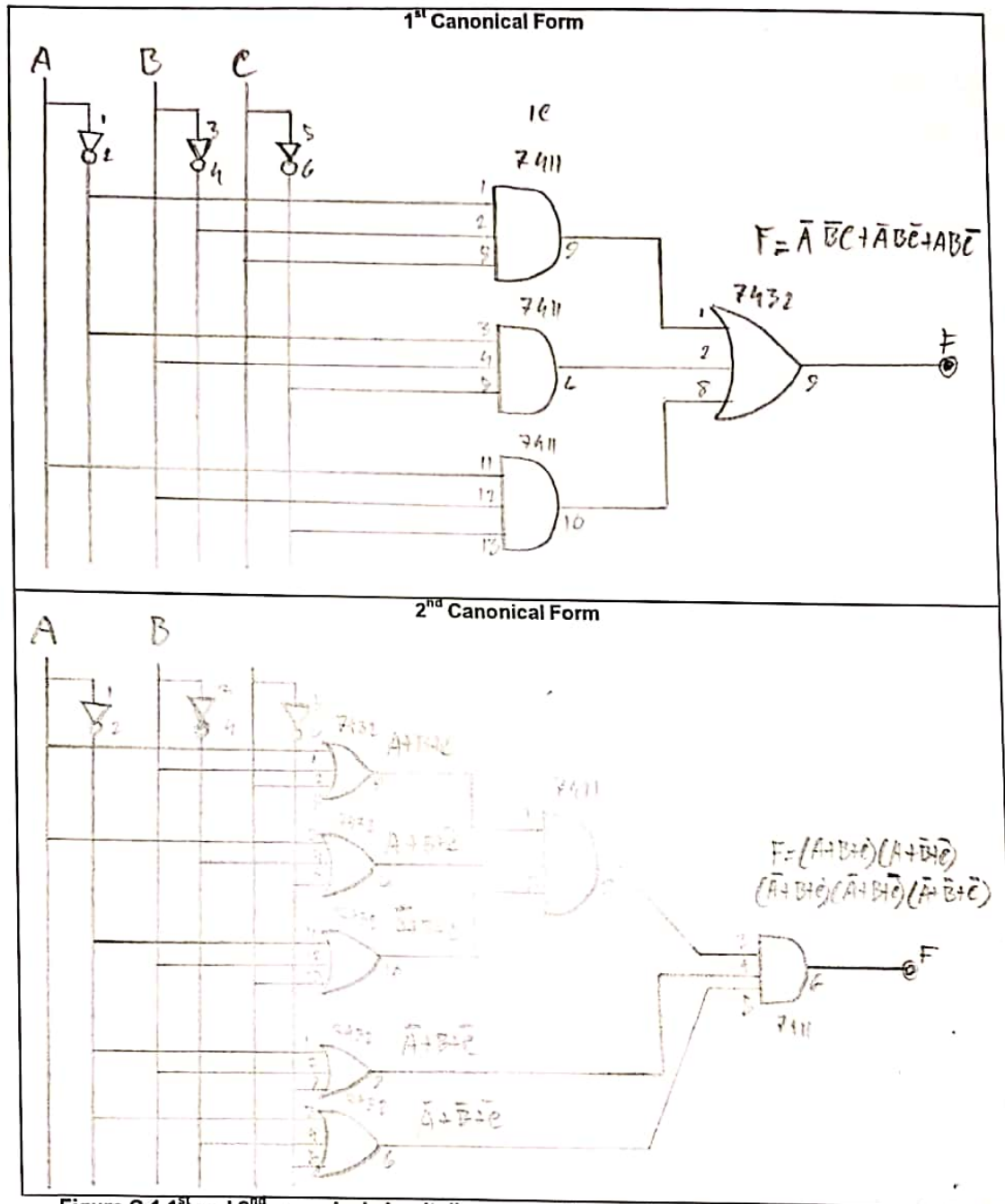


Figure C.1 1<sup>st</sup> and 2<sup>nd</sup> canonical circuit diagrams of the combinational circuit of Table C.1

4. Construct the 1<sup>st</sup> canonical form of the circuit and test it with the truth table.
  - i. Connect one min term at a time and check its output.
  - ii. Once all min terms have been connected and verified, OR the min terms for the function output.

### C.3. Report

Simulate above two circuits (1<sup>st</sup> and 2<sup>nd</sup> canonical forms) in Logisim.

Prithika  
13/3/24